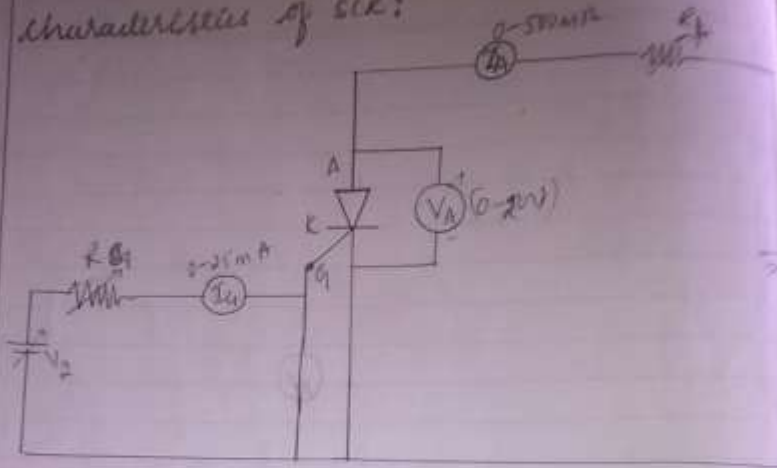


Characteristics of SCR:



Tabular Column:

$I_{G1} = 10.2 \text{ mA}$; $I_{G2} = 17.7 \text{ mA}$

$I_{G1} = I_{G2} = 10.2 \text{ mA}$		$I_{G2} = 17.7 \text{ mA}$	
V_{AK}	$I_A (\text{mA})$	V_{AK}	$I_A (\text{mA})$
0.2	49	0.2	12
0.2	64	0.3	39
0.3	81	0.4	71
0.4	96	0.5	88
0.5	118	0.6	122
0.6	165	0.7	149
0.7	203	0.8	200
0.8	253	0.8	219
0.9	290	0.8	277

STATIC CHARACTERISTICS OF SCR

Date: _____

Page No: 1

Aim: To plot the characteristics of an SCR & to find the forward resistance, holding current & latching current

Apparatus:

1. SCR TYN616 - 1
2. DC voltmeter & ammeter - 1 each
3. Rheostat

Procedure:

V-I characteristics

- a. Make the connections as given in theckt. dig including meters for I_{T1} , TYN 616
- b. Keep V_{AK} & V_{GK} potentiometer at minimum voltage position & at off position.
- c. Keep load potentiometer R_L at maximum position & gate potentiometer R_g at maximum resistance position.
- d. Switch ON the main supply to the unit.
- e. Switch ON anode supply - V_{AK} & set at 10V.
- f. Switch ON the gate supply.
- g. slowly vary voltage V_{GK} till the SCR turn ON. This can be noticed by sudden increase in $I_c = I_a$ & sudden drop of V_{AK} to 0.6V. This gate current is the I_g to turn ON. Increase the I_g by reducing R_g . If the I_g is below I_{gmin} the SCR does not even turn ON even if the anode voltage increased.

S.D.M. JAINMATT NAVAGRAHATEERTH TRUST (R.)

A.G.M.R. COLLEGE OF ENGINEERING AND TECHNOLOGY, VARUR

Scanned with CamScanner

Observations :


$$I_{q1} = 10.2 \text{ mA}$$


$$I_{q2} = 17.7 \text{ mA}$$


$$\text{Latching current} = I_L = 29 \text{ mA}$$


$$\text{Holding current} = I_H = 16 \text{ mA}$$

Nature of graph:

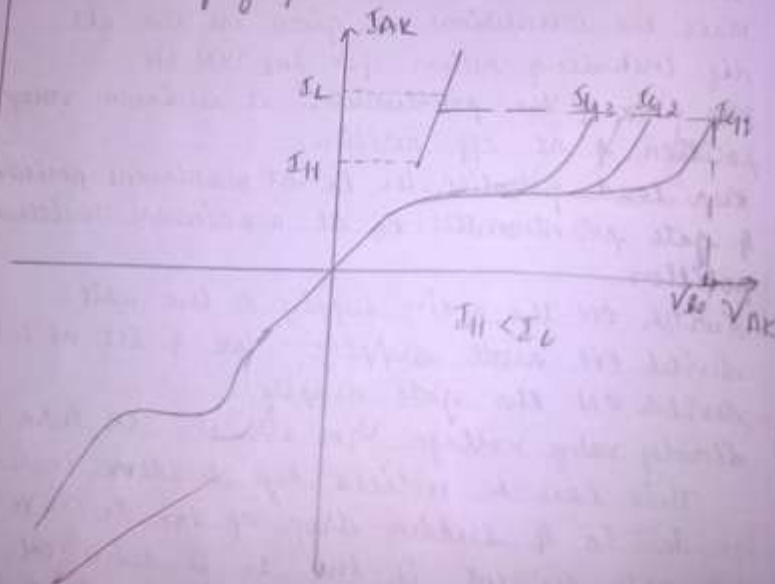


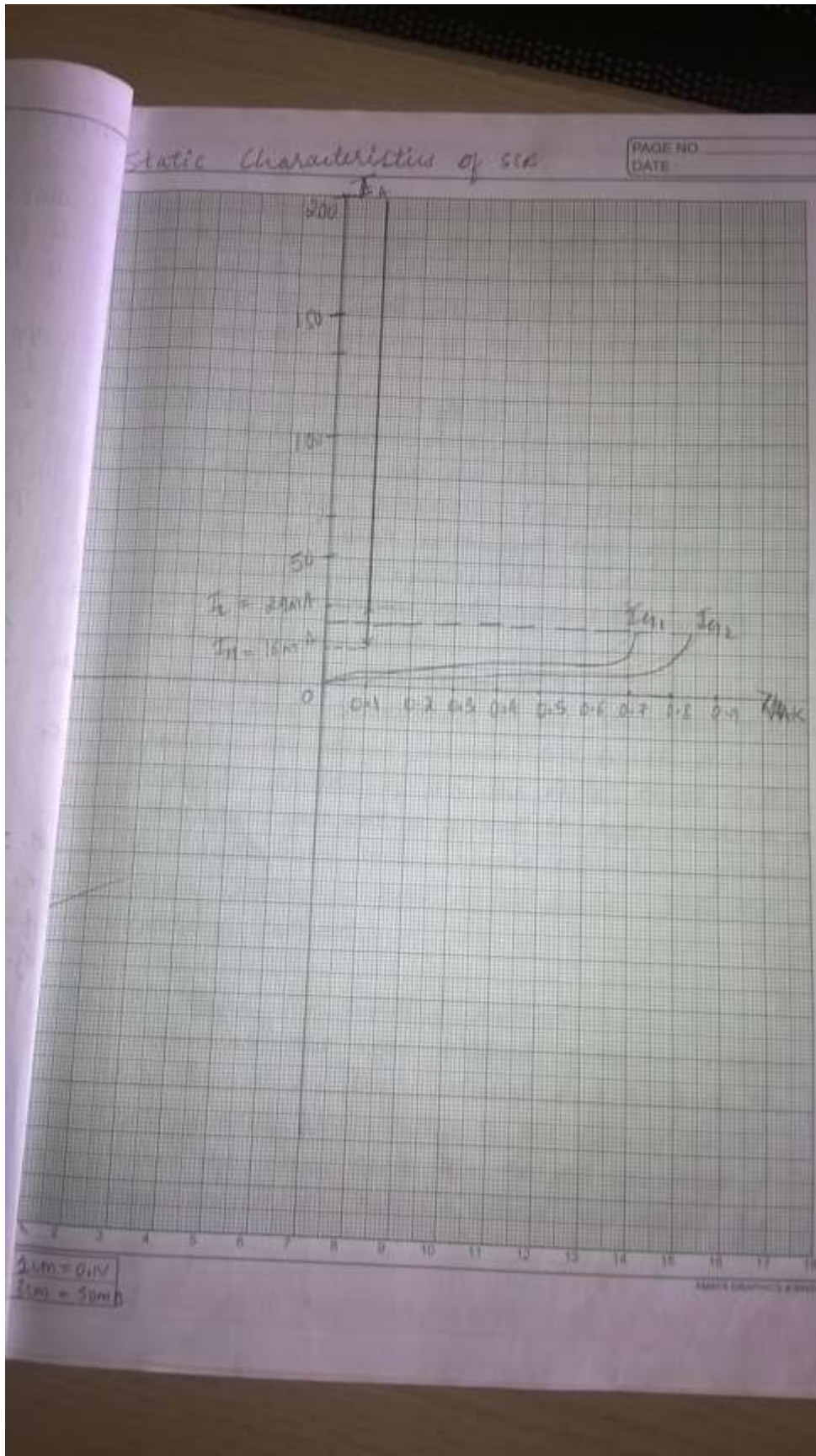

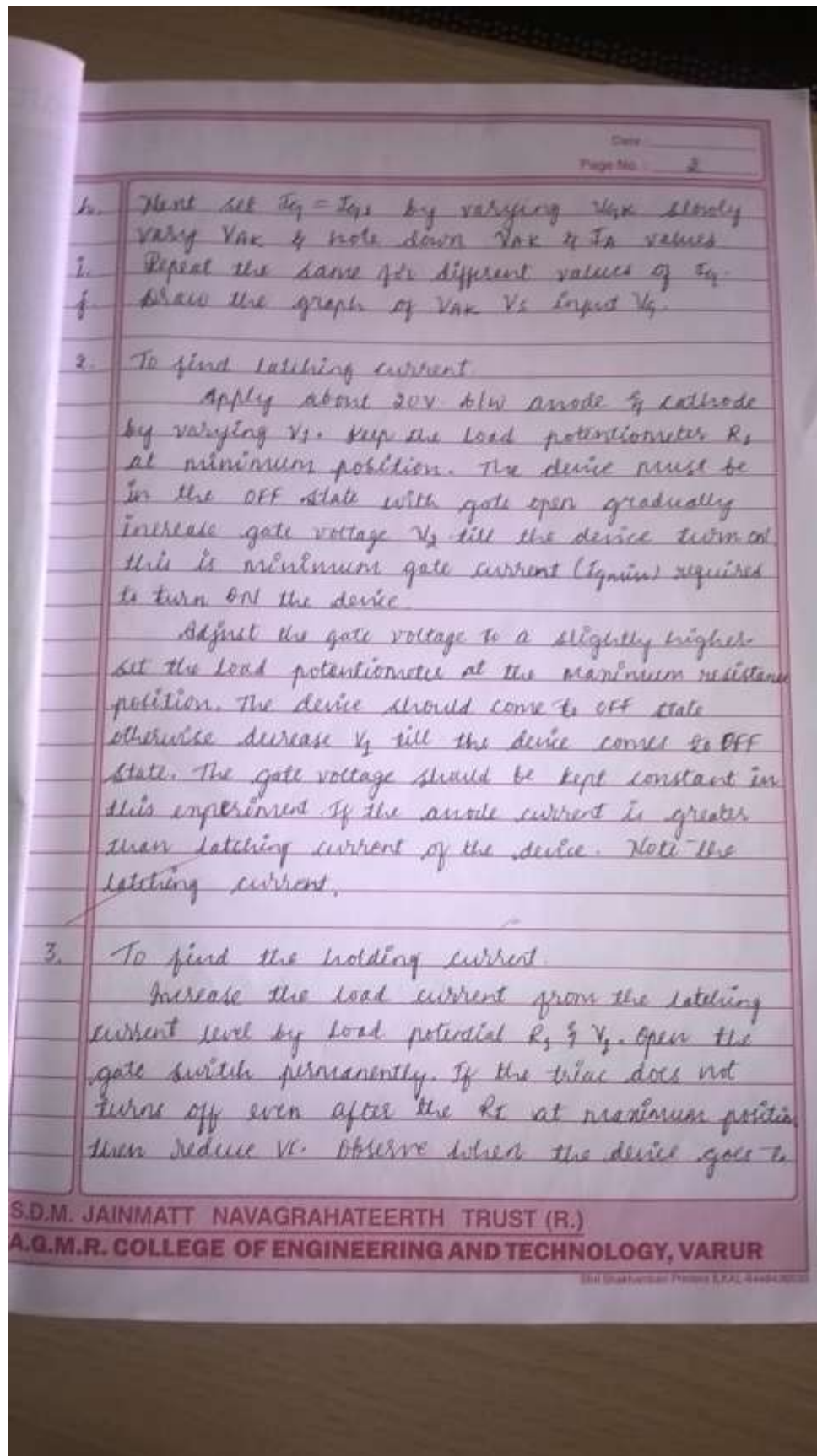

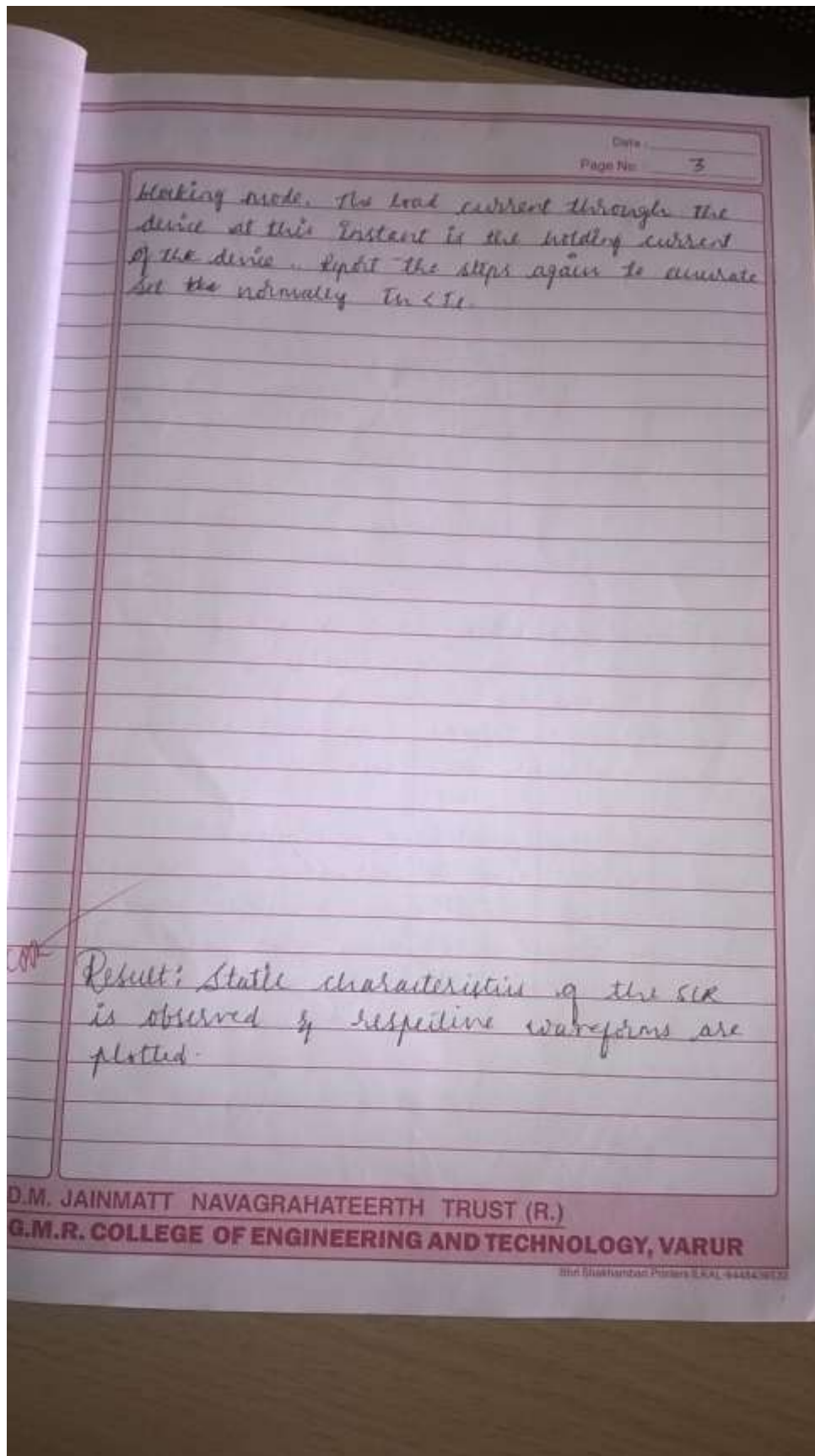

Characteristics of MOSFET

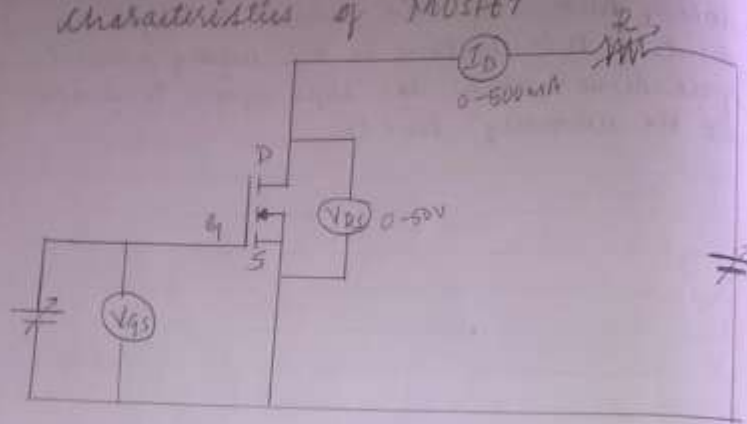

Tabular Column

$V_g = V_{ds} = 1.0V$	
$V_{gs}(V)$	$I_D(mA)$
2.88	0.001
3.11	0.009
3.15	0.012
3.22	0.018
3.24	0.025
3.30	0.027
4.50	0.027

STATIC CHARACTERISTICS OF MOSFET AND IGBT

Date: _____
Page No: 4

Aim: To study the characteristics of MOSFET and IGBT.

Apparatus:

- | Sl. No | Components |
|--------|-------------------------|
| 1 | External Meter |
| 2 | Connecting wire, probes |
| 3 | IGBT/MOSFET Module |


MOSFET


Procedure:


1. Transconductance characteristics
- Make the connections as shown in the ckt diagram with meters
 - Initially keep V_d & V_s zero, set $V_g = V_{gs}$ [say 10V]
 - Slowly vary V_g [V_{gs}] & note down I_d & V_{gs} readings for every 0.5V and enter in the tabular column
 - Repeat the same procedure for different voltage values of $V_d = V_{ds}$ and note down the readings.

The minimum gate voltage V_{gs} which is required for conduction to start in the MOSFET is called threshold voltage $V_{gs(th)}$. If V_{gs} is less than $V_{gs(th)}$, only small leakage current flows from drain to source. If V_{gs} is greater than $V_{gs(th)}$, the drain current depends on magnitude of the gate voltage V_{gs} varies from 2 to 5 volts.

- Plot the graph I_d Vs V_{gs}

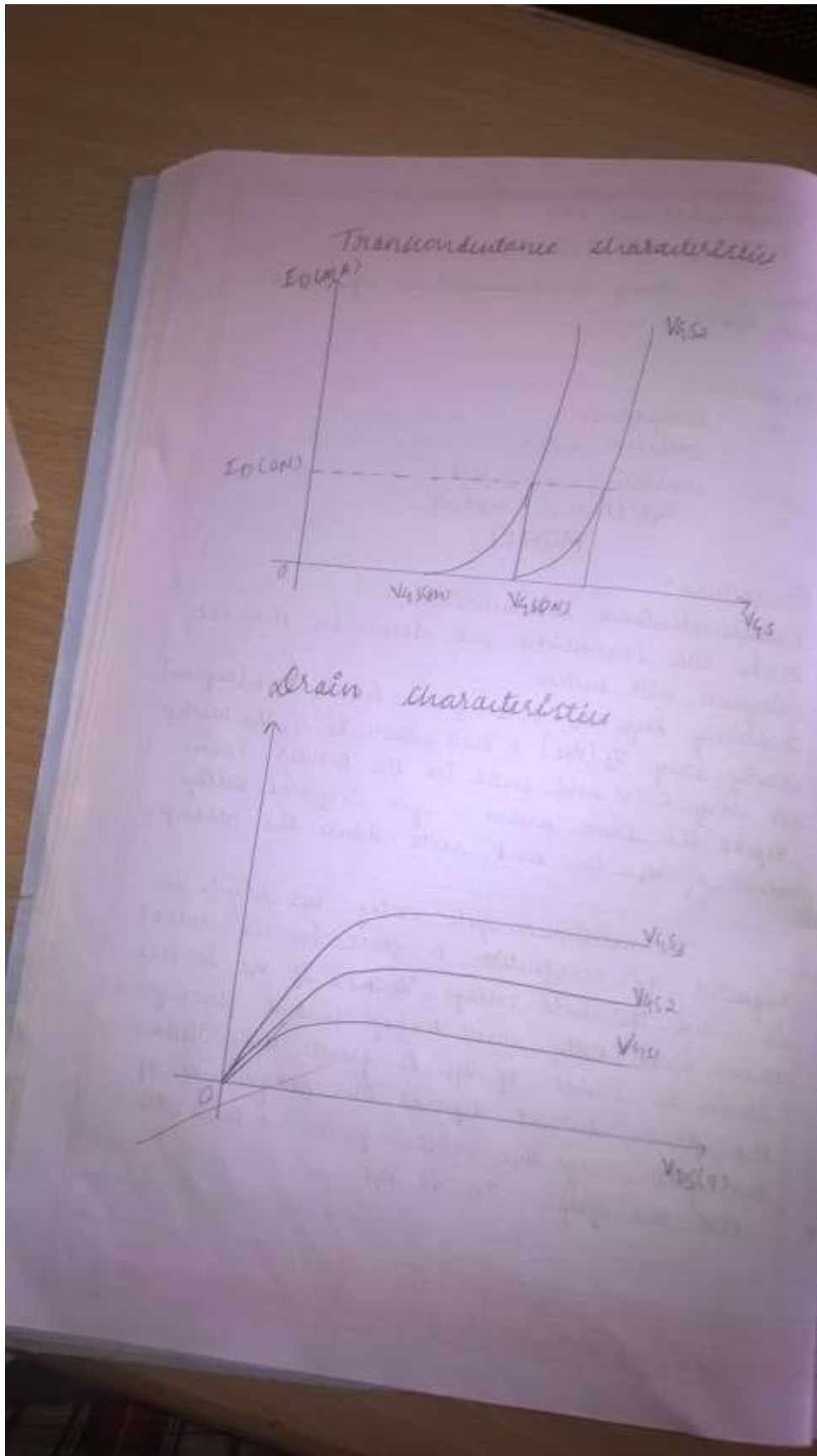

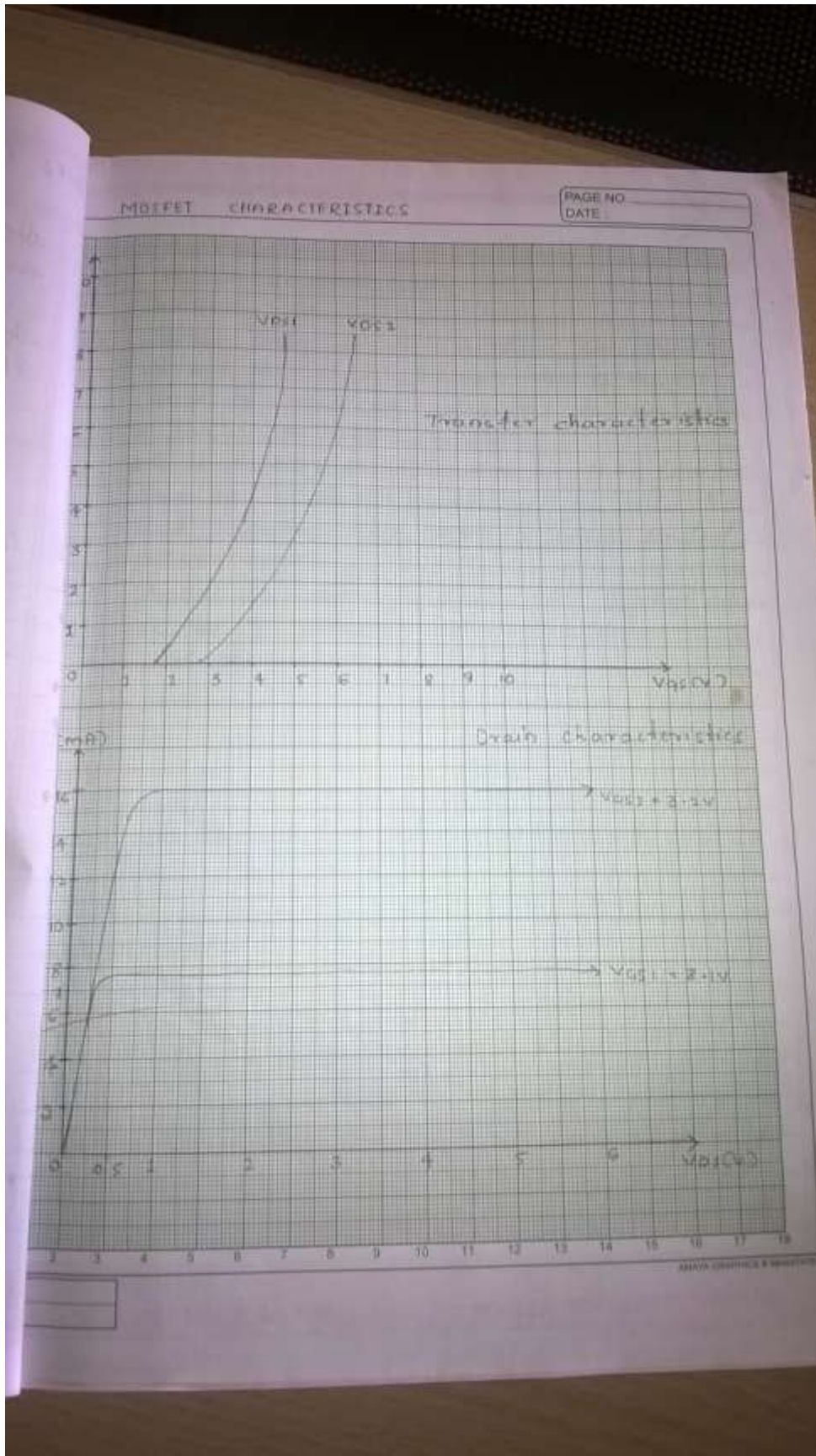


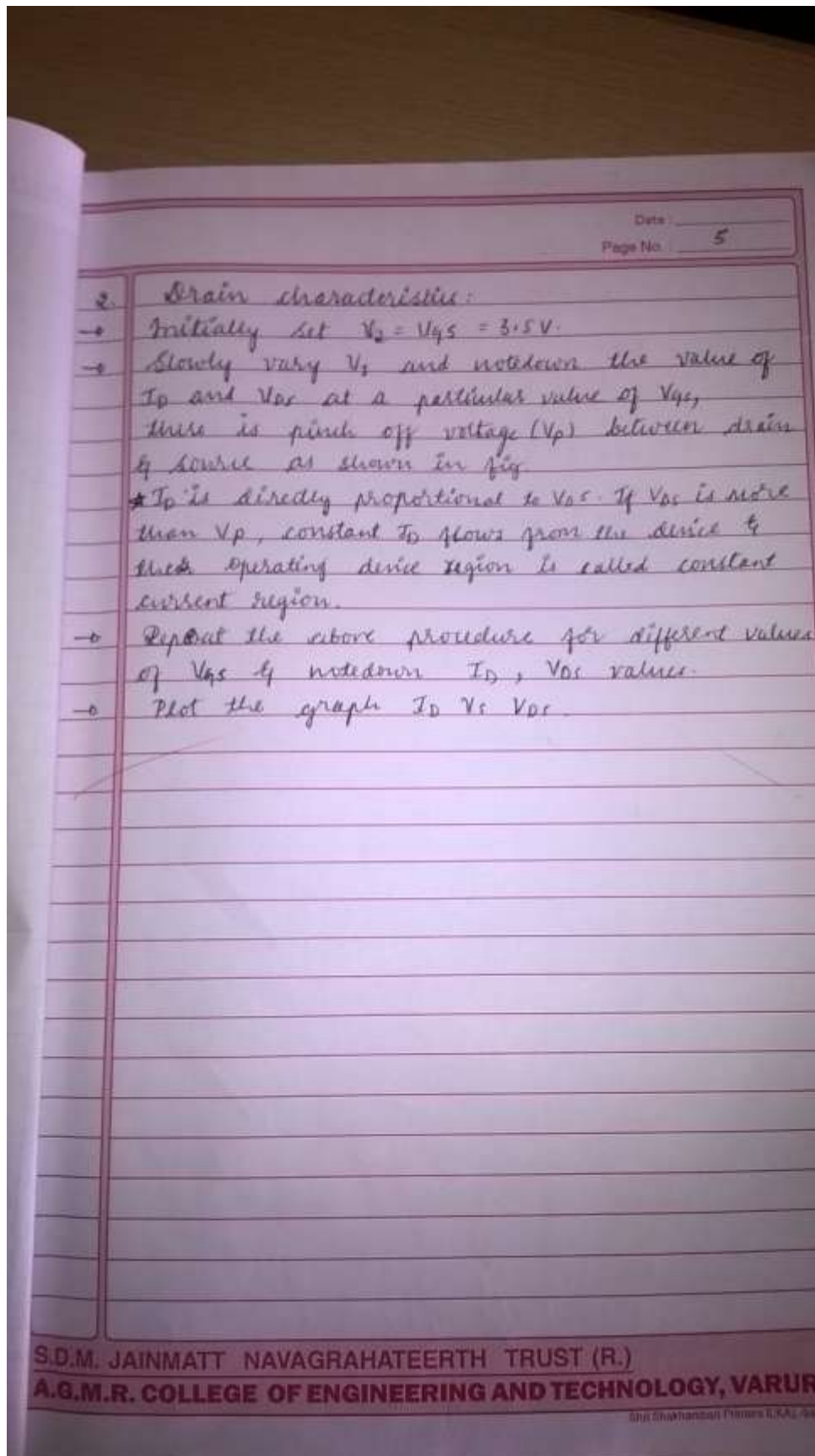


Tabular Contents
Drain Characteristics


$V_{GS} = V_{DS} = 3.5V$		$V_{GS} = V_{DS} = 3.55V$		$V_{GS} = V_{DS}$
$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$
0.1	0.059	0.1	0.037	0.3
0.2	0.057	0.2	0.062	0.4
0.3	0.066	0.3	0.072	0.5
0.4	0.074	0.4	0.081	0.6

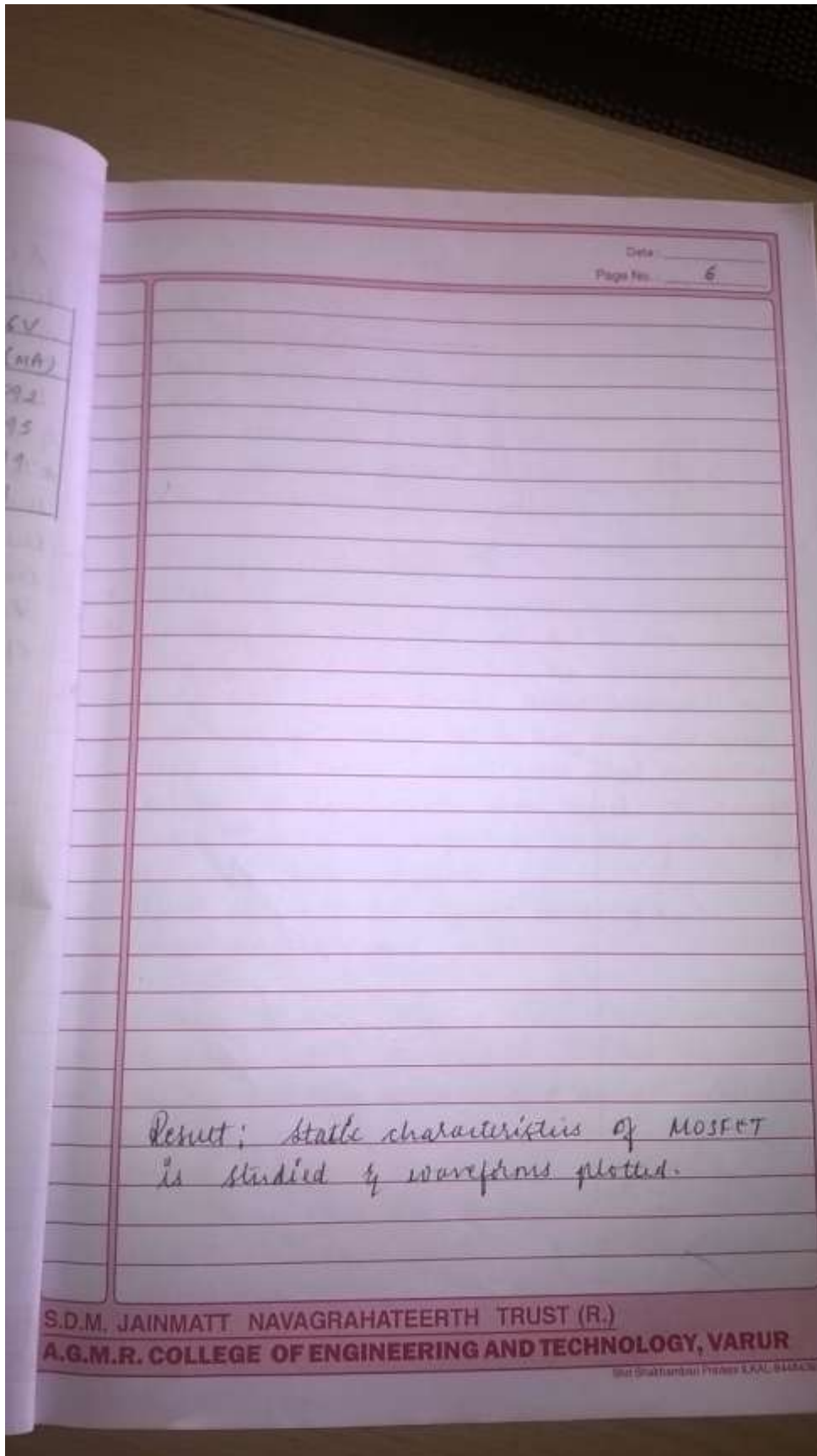
[Faint handwritten notes and diagrams are visible below the table, but they are illegible due to blurriness.]




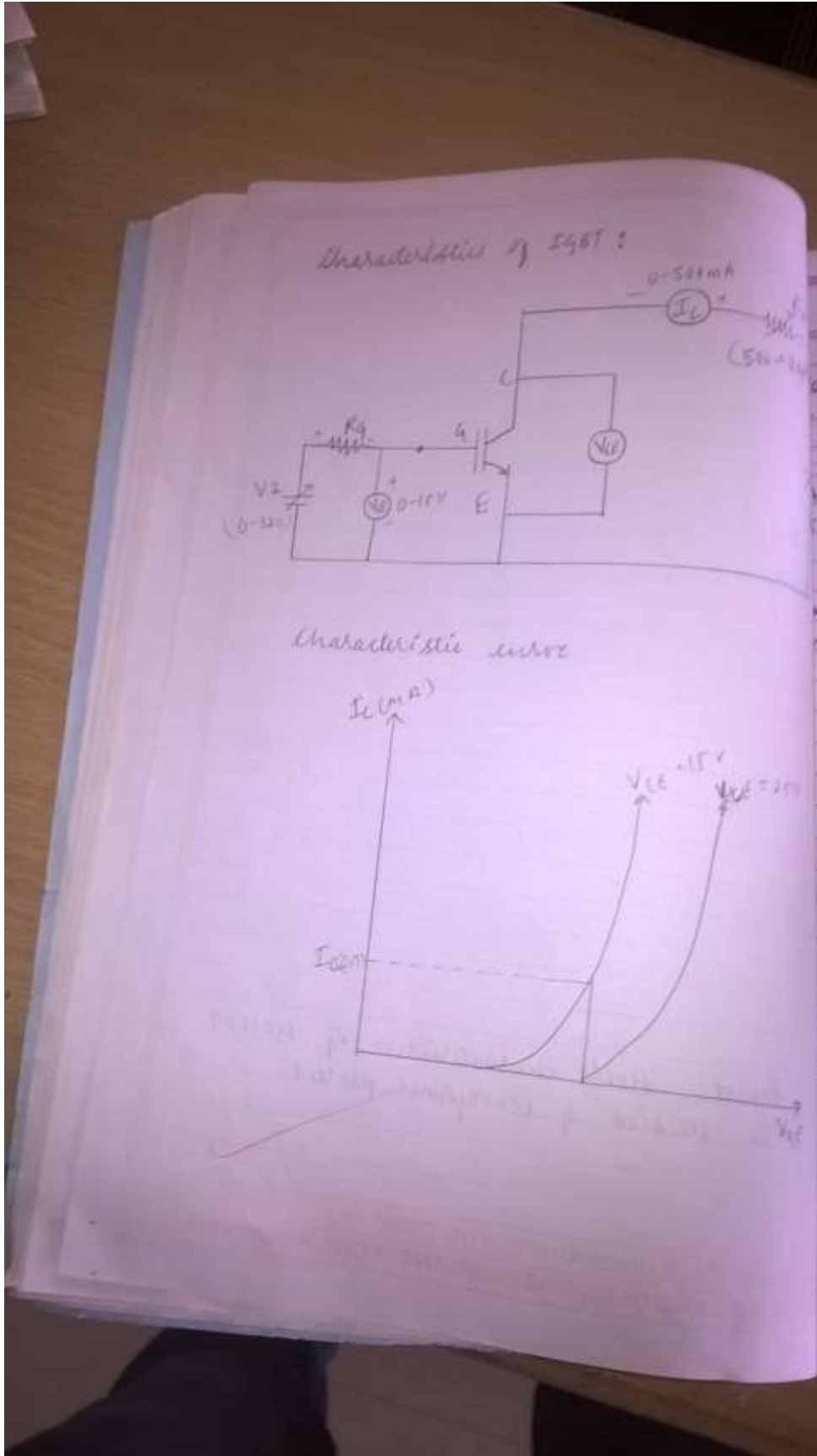
Result: static characteristics of MOSFET
is studied & waveforms plotted.




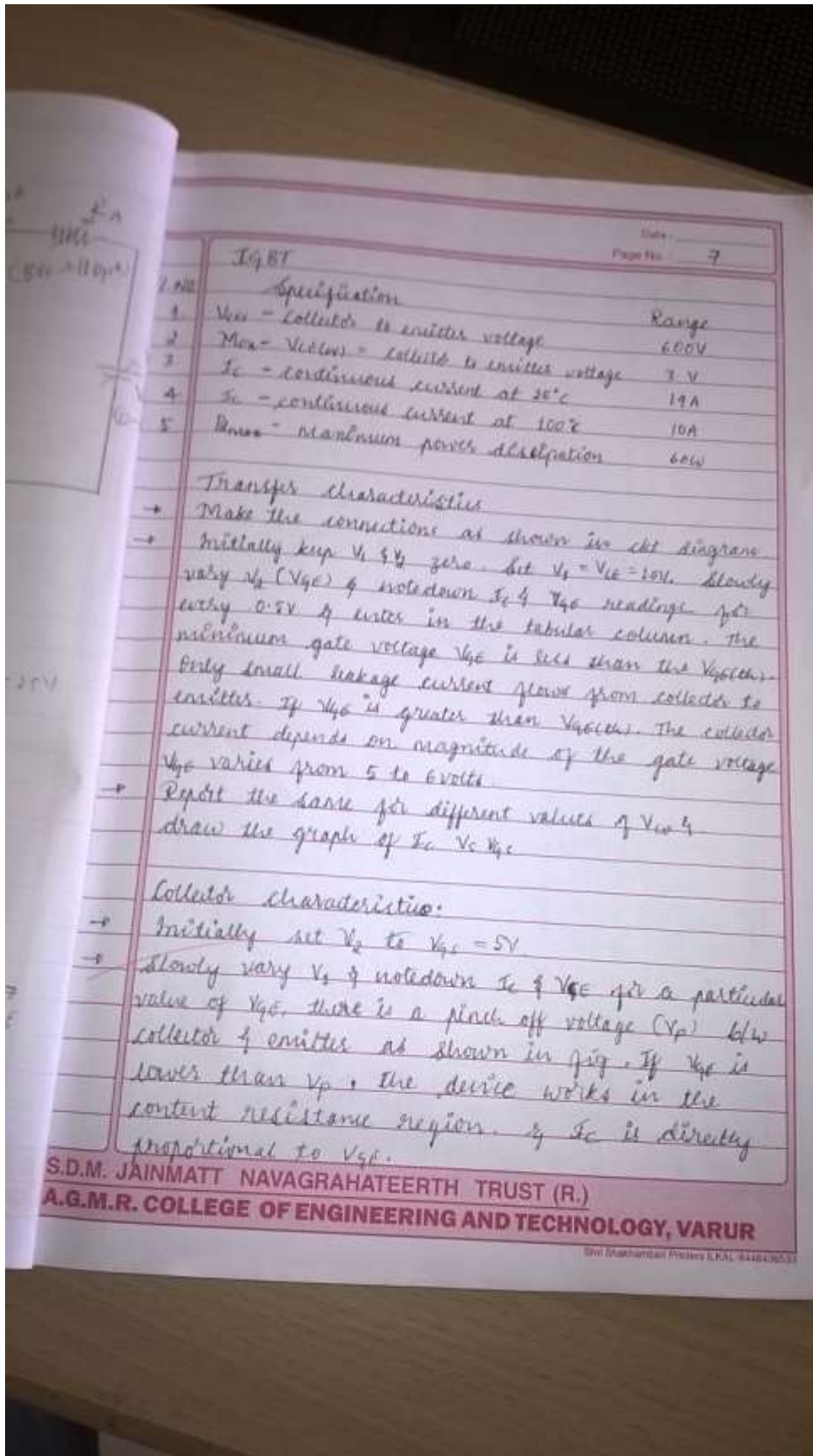


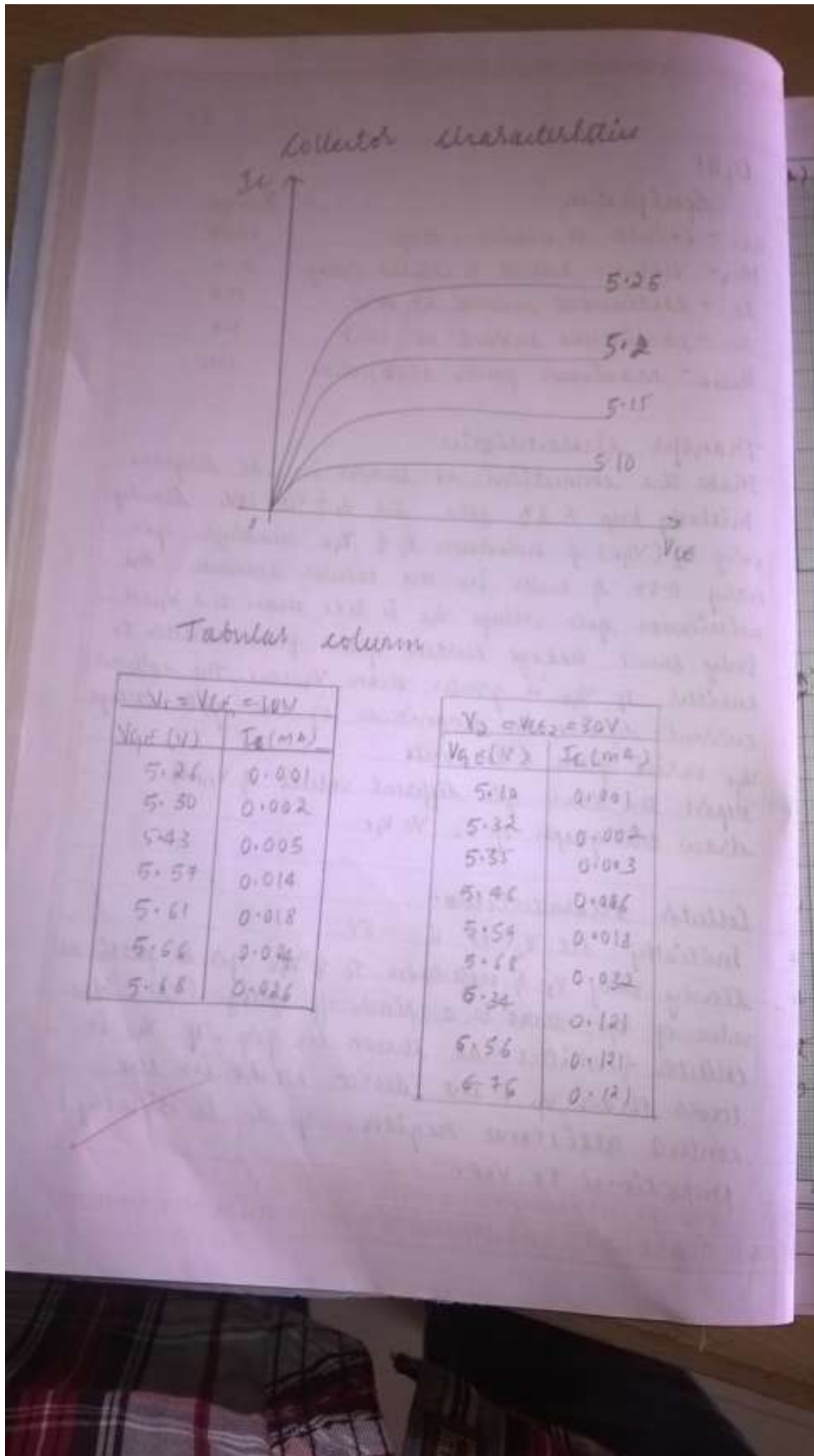


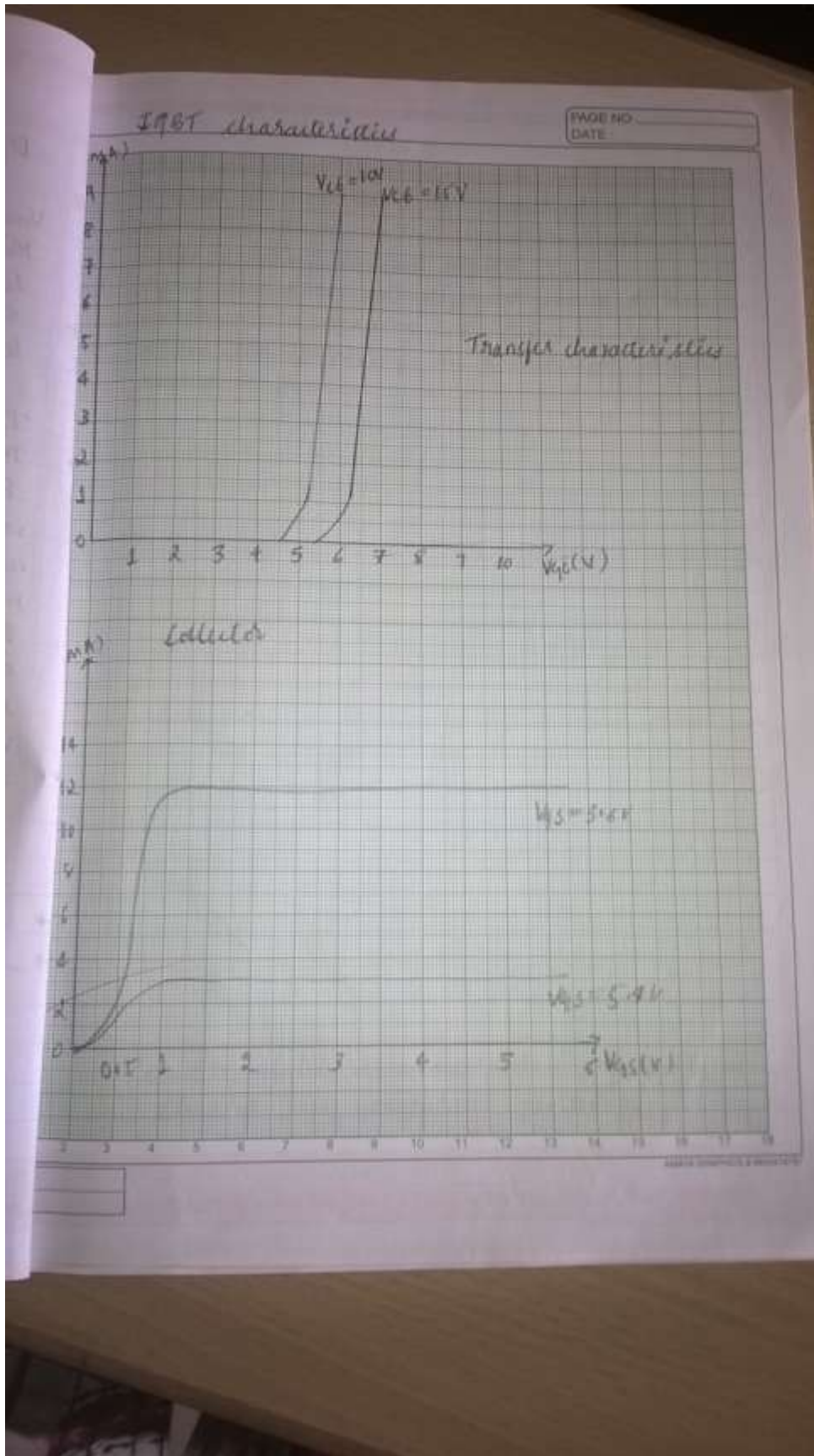


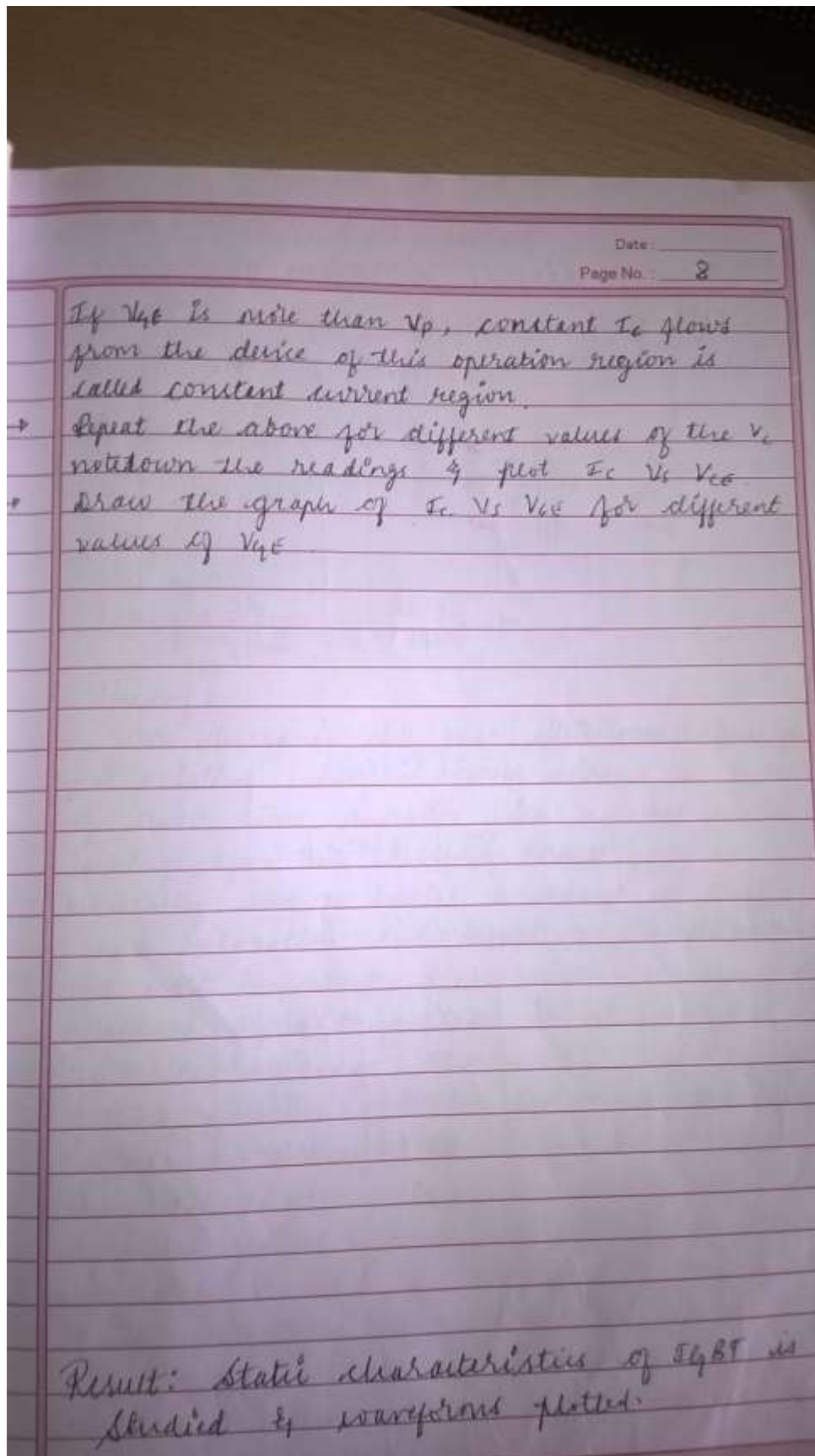

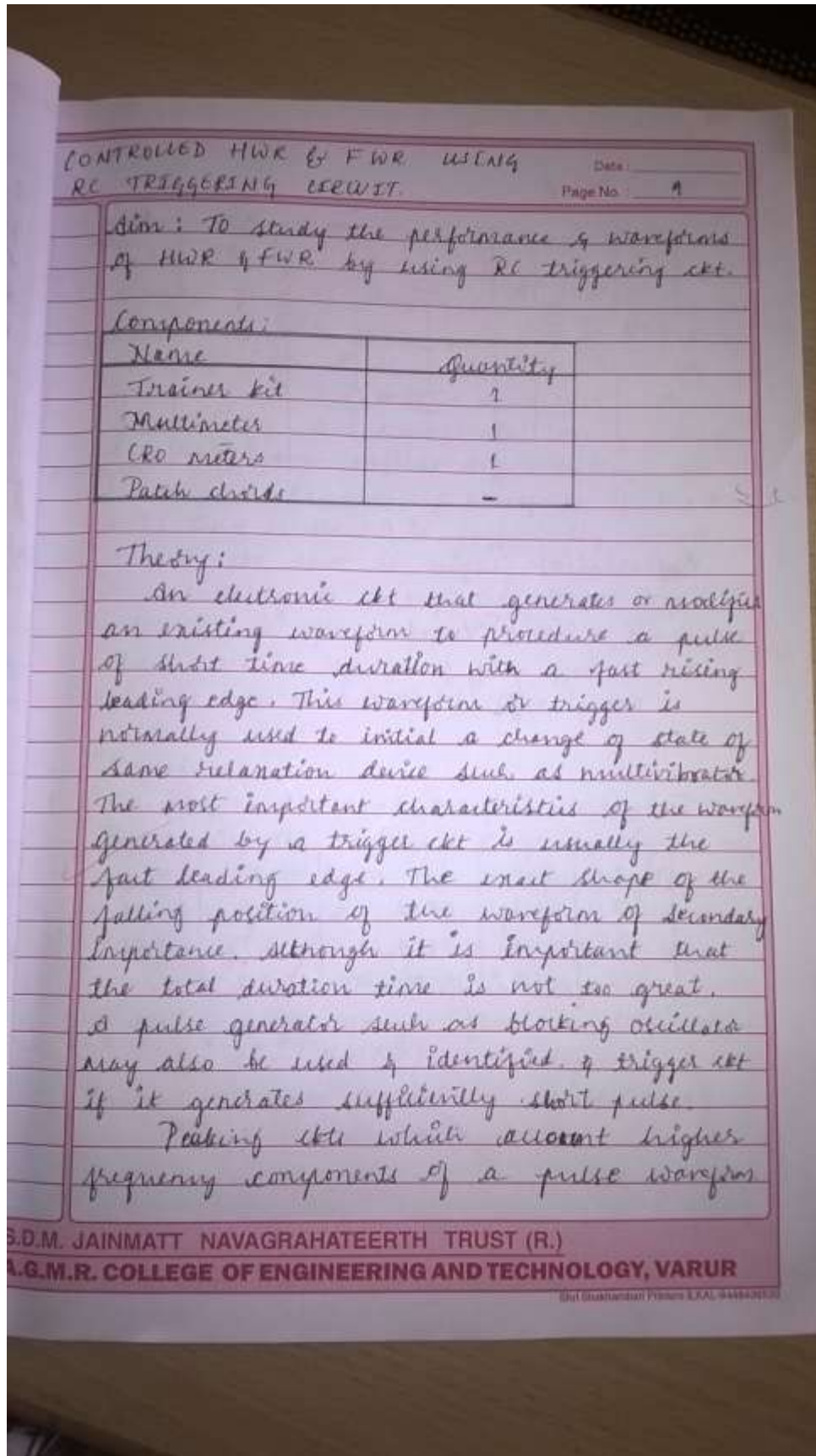


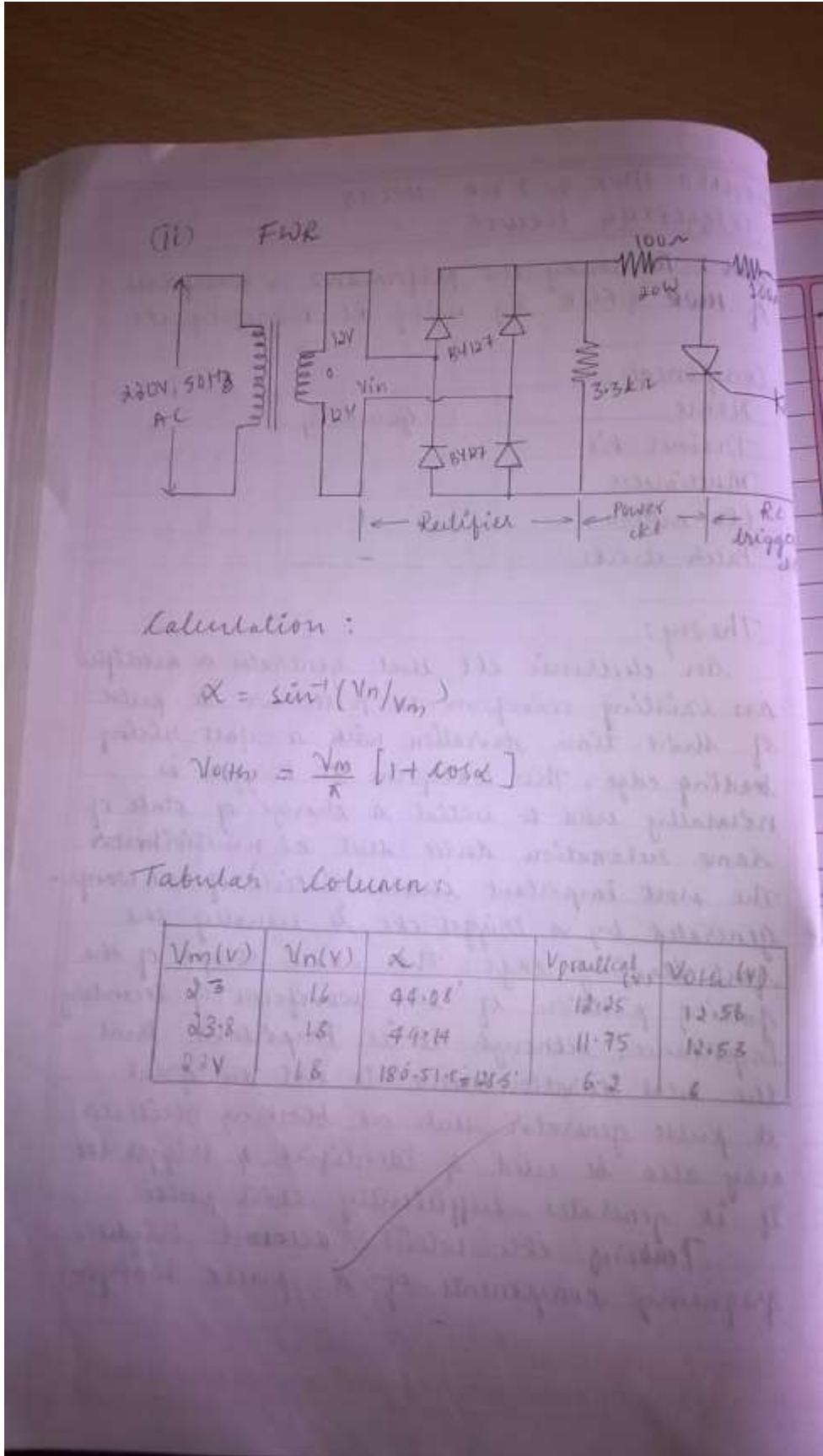

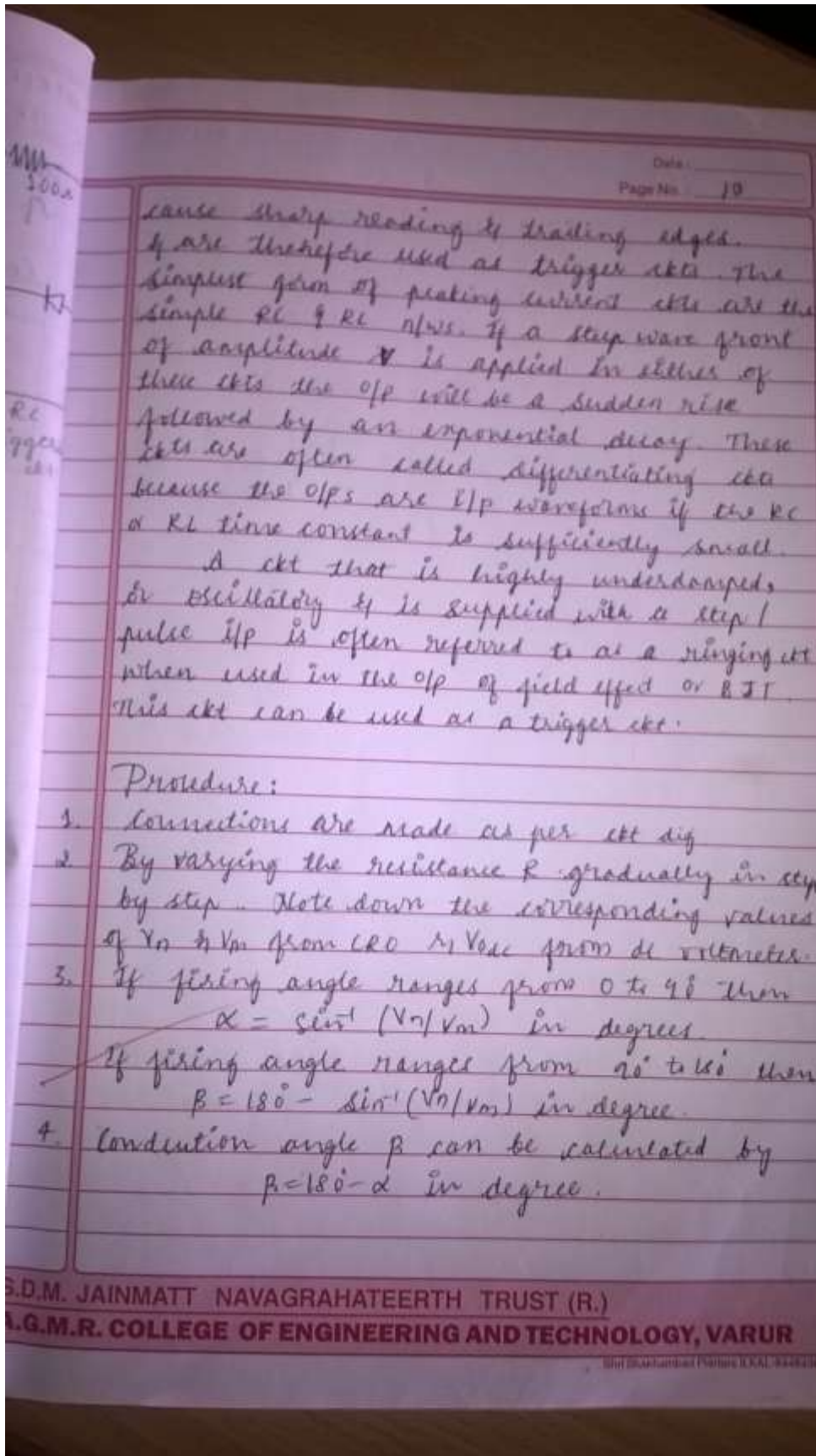

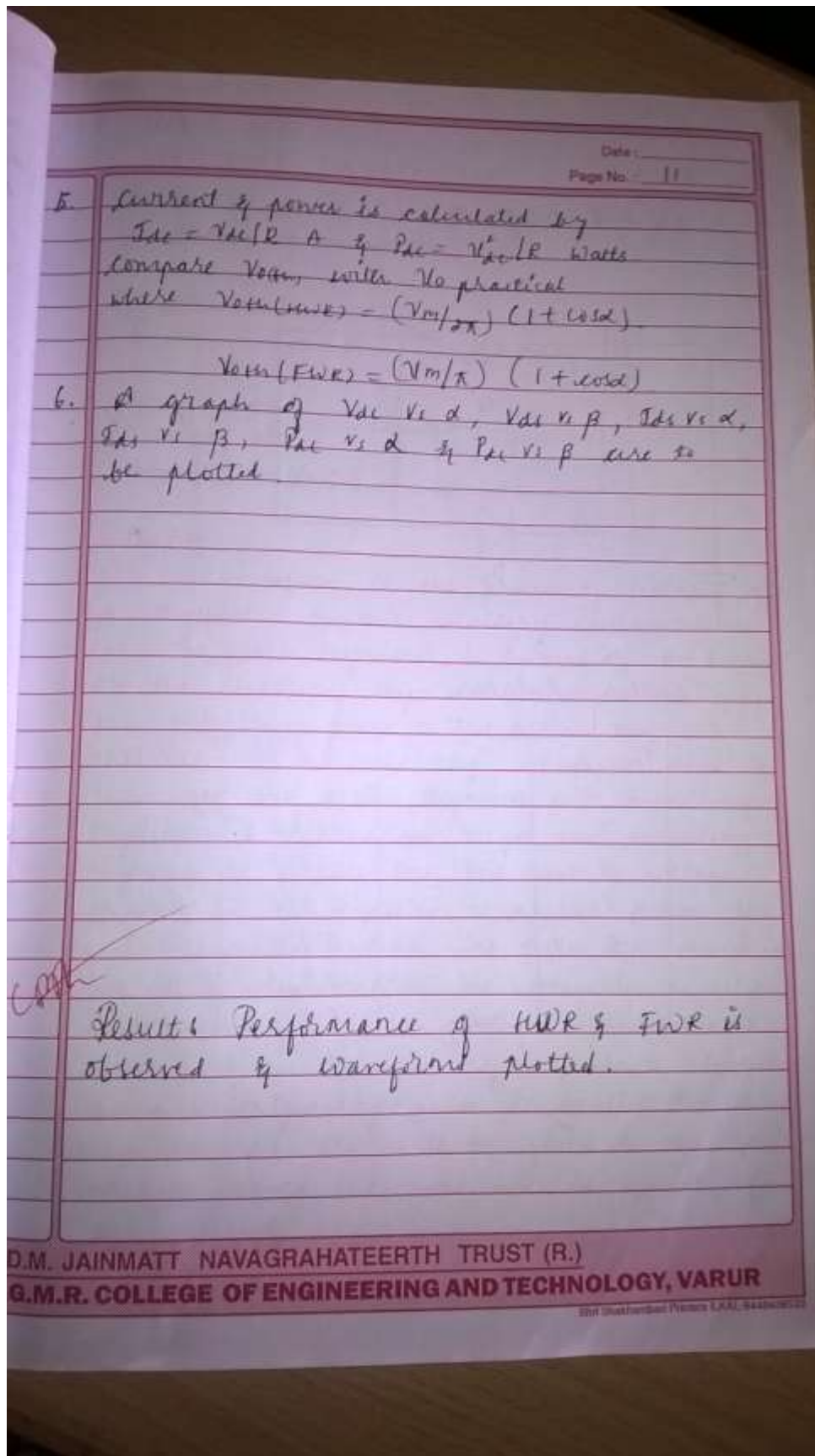



Circuit Diagram

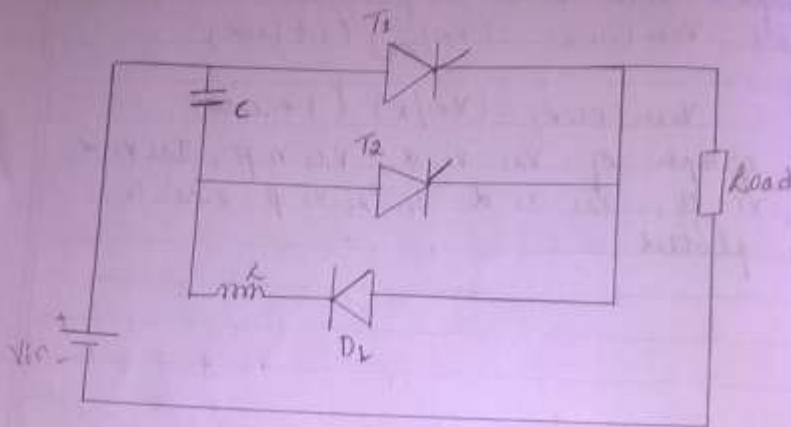

Tabular Column:

$T_{on}(k\mu s)$ in ms	$T_{off}=T$ ms	$k = \frac{T_{on}}{T}$	$V_o(V)$
3	21	0.142	3.1
5	21	0.238	4.6
6	21	0.285	6.3
8	21	0.380	8.0
10	21	0.476	10.1
32	21	0.571	12.1

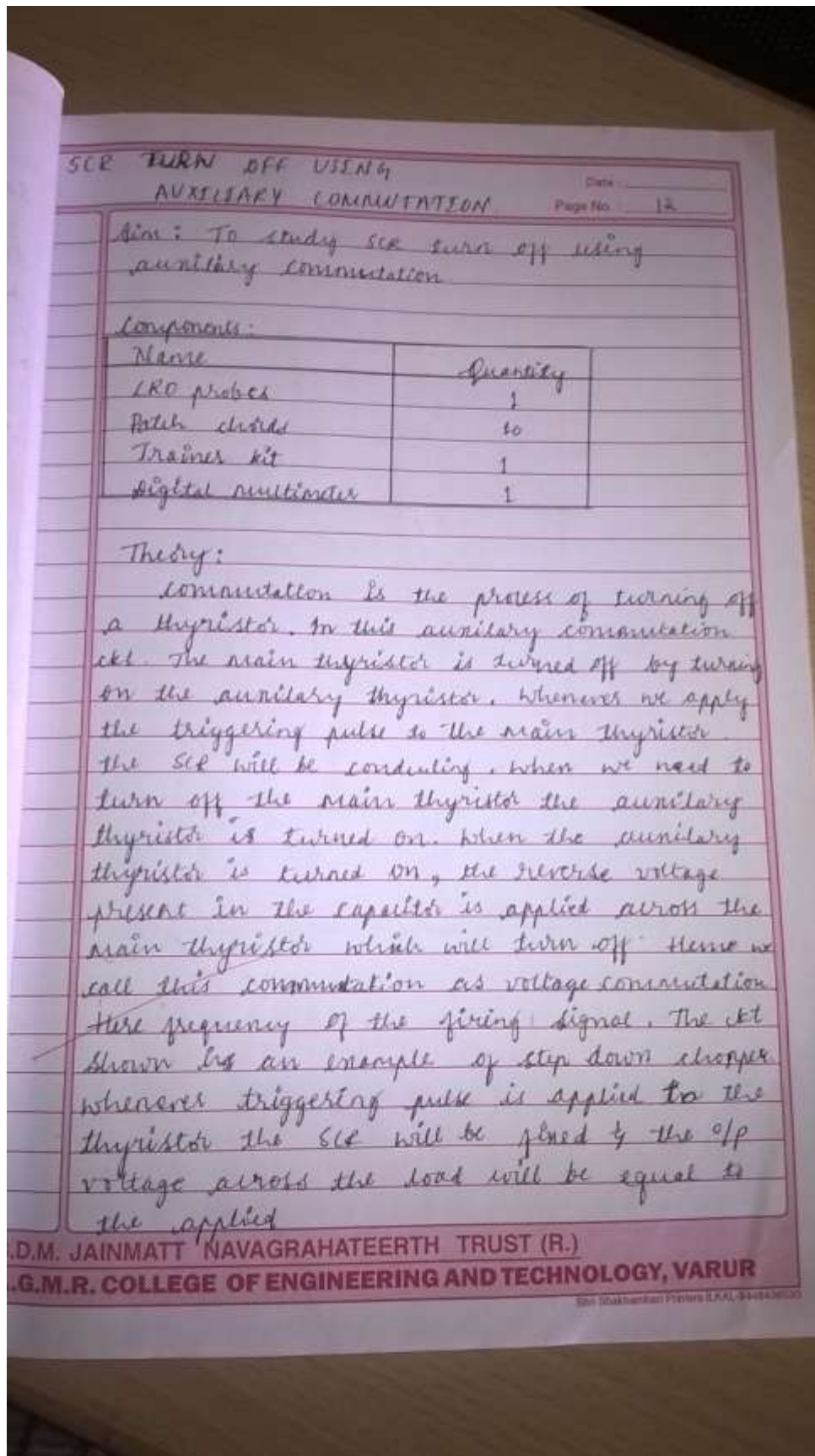

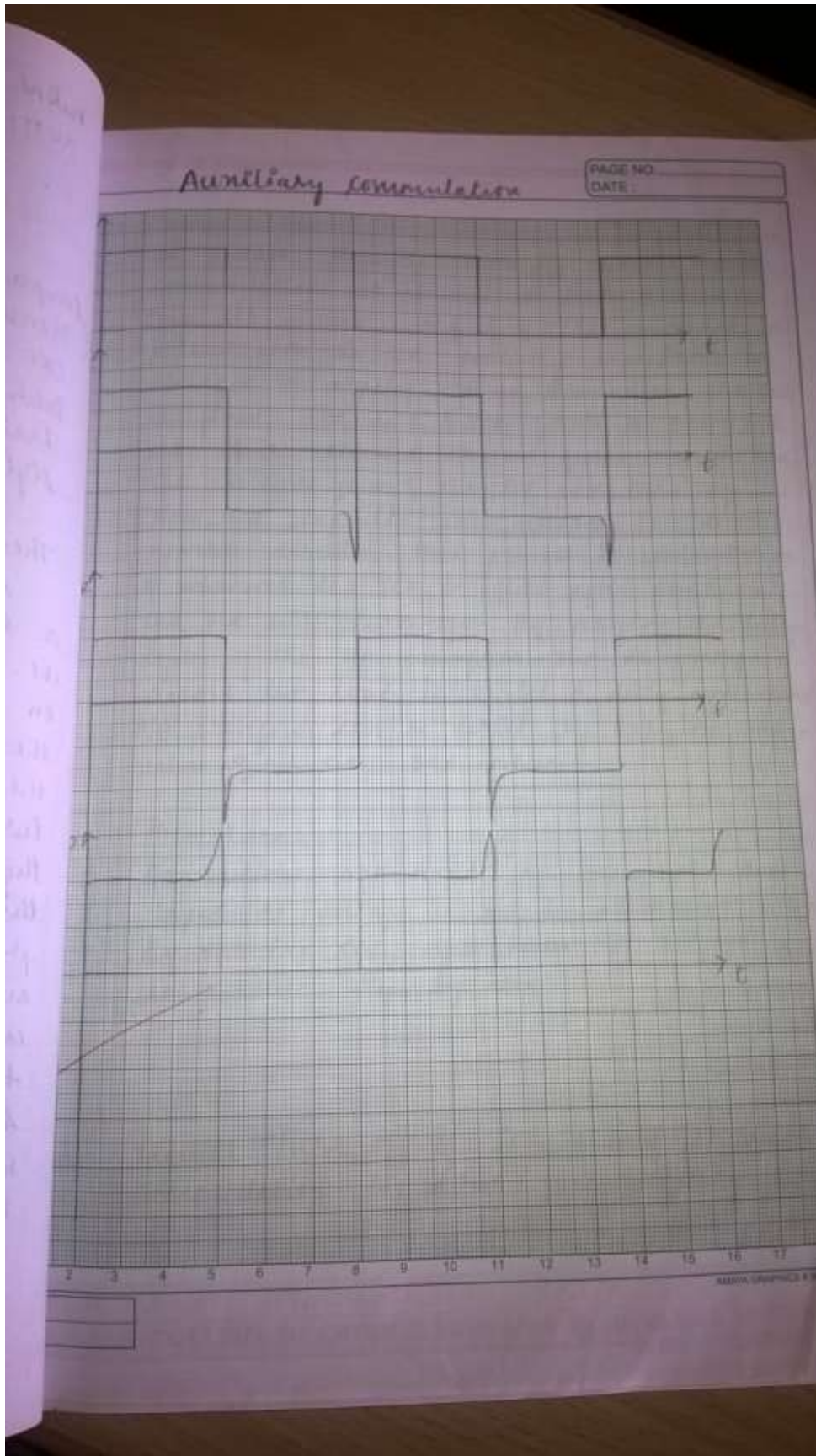

Date: _____

Page No. 13


dc voltage. Now to turn off the SCR an LC commutation ckt is used. A series resonant tank ckt formed using L & C is connected in parallel with the SCR. Initially capacitor is charged to supply voltage 'V'. When the SCR is fired. The L, C & SCR forms a resonant ckt & a resonant current flows through the SCR becomes zero & the SCR will turn off. Now the capacitor will charge in series, reverse direction. This process is commutative & whenever the SCR is fired after some time the SCR will turn off. By varying the duty cycle of the off waveform, the dc voltage across the load is varied & duty cycle of the off waveform can be varied by varying the value of L, C or DRB values.

Procedure:

1. Connections are made as per ckt diag.
2. Input dc voltage is set to convenient value
3. By varying duty cycle knob of triggering ckt module slip by slip.

Result: Turn off of SCR using auxiliary commutation is done successfully.

Circuit Diagram

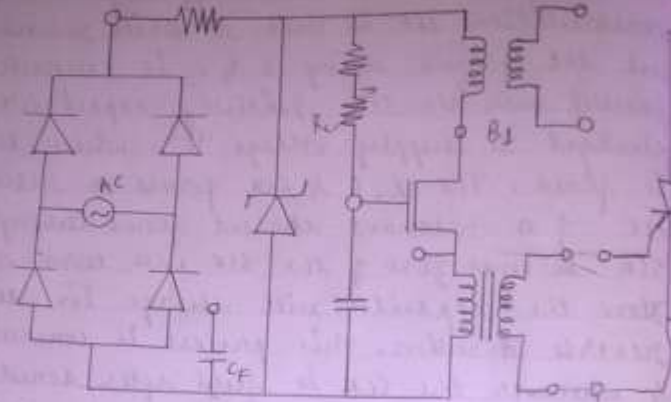

Tabular Solution:


[i] 0 to 90°

$V_o (V)$	$V_m (V)$	α°	β°	$V_{om} (A)$	$V_{pr} (A)$
16.2	30.4	30	150	18.05	16.2
16.4	30.10	37.68	142.31	17.76	16.2
18.5	30.49	20.14	159.86	12.21	16.3
15	30.10	26.53	153.41	15.17	17.4

where $\alpha = \sin^{-1} (V_o / V_m)$

$\beta = 180^\circ - \alpha$

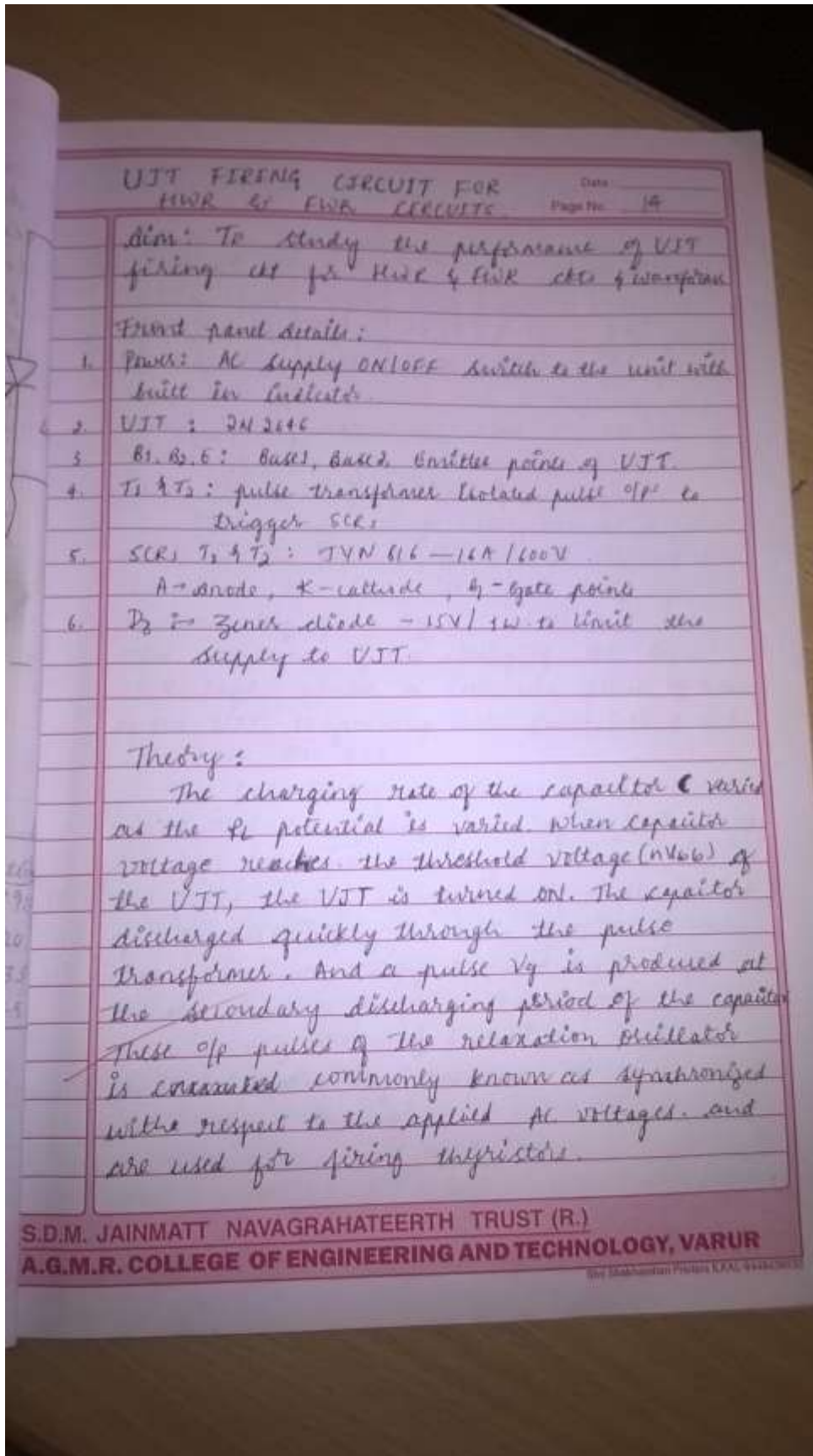$V_o (AV) = \frac{V_m}{\pi} [1 + \cos \alpha]$



[ii] 90° to 180°

$V_n(V)$	$V_m(V)$	α°	β°	$V_{ohm}(V)$	$V_{pract}(V)$
20	30.10	41.60	138.4	16.74	19.23
17	28.10	76.64	103.35	12.5	14.20
15	30.44	66.68	113.31	13.54	15.15

where $\alpha = 180 - \sin^{-1} [V_n/V_m]$

$$\beta = 180 - \alpha$$

$$V_{ohm} = \frac{V_m}{n} [1 + \cos \alpha]$$

